


Digital Integrated Circuits
A Design Perspective
Prentice Hall Electronics and VLSI Series
ISBN 0-13-120764-4

The Inverter

[Adapted from Rabaey's *Digital Integrated Circuits*, Second Edition, ©2003
J. Rabaey, A. Chandrakasan, B. Nikolic]
Copyright 2003 J. Rabaey et al.


Inverter

The CMOS Inverter: A First Glance

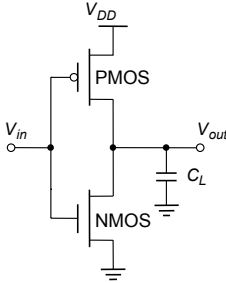

Inverter


CMOS Inverter
First-order DC Analysis

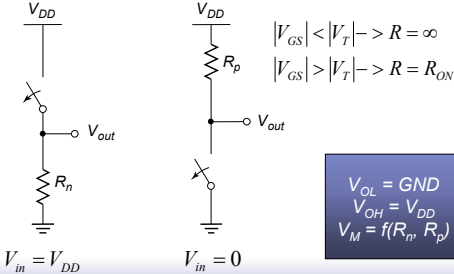


$V_{OL} = GND$
 $V_{OH} = V_{DD}$
 $V_M = f(R_n, R_p)$

Inverter

CMOS Inverter: Transient Response

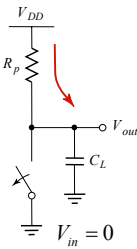

(a) Low-to-high

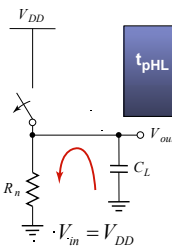

(b) High-to-low


$$t_{pHL} = f(R_{on} \cdot C_L) = 0.69 R_{on} C_L$$

Inverter

CMOS Properties

- Full rail-to-rail swing \Rightarrow high noise margins
 - Logic levels not dependent upon the relative device sizes \Rightarrow transistors can be minimum size \Rightarrow ratioless
- Always a path to V_{dd} or GND in steady state \Rightarrow low output impedance (output resistance in $k\Omega$ range) \Rightarrow large fan-out (albeit with degraded performance)
- Extremely high input resistance (gate of MOS transistor is near perfect insulator) \Rightarrow nearly zero steady-state input current
- No direct path steady-state between power and ground \Rightarrow no static power dissipation
- Propagation delay function of load capacitance and resistance of transistors






Inverter

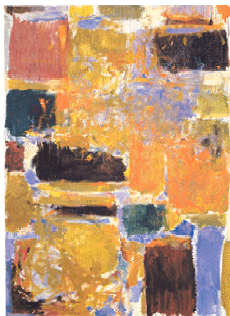


Voltage Transfer Characteristic

Inverter



     

 CMOS Inverter:
Switch Model of Dynamic Behavior



Gate response time is determined by the time to charge C_L through R_p (discharge C_L through R_n)

Inverter

Relative Transistor Sizing

- When designing static CMOS circuits, balance the driving strengths of the transistors by making the PMOS section wider than the NMOS section to
 - maximize the noise margins and
 - obtain symmetrical characteristics

Inverter

Switching Threshold As a
Function of Transistor Ratio

V_M where $V_{IN} = V_{OUT}$ (both PMOS and NMOS in saturation since $V_{GS} = V_{DS}$)

Velocity-Saturation $V_{DSAT} < V_M - V_T$

$$I_{Dn} + I_{Dp} = 0$$

$$k_n V_{DSATn} \left(V_M - V_{Tn} - \frac{V_{DSATn}}{2} \right) + k_p V_{DSATp} \left(V_M - V_{DD} - V_{Tp} - \frac{V_{DSATp}}{2} \right) = 0$$

$$V_M = \frac{\left(V_{Tn} + \frac{V_{DSATn}}{2} \right) + r \left(V_{DD} + V_{Tp} + \frac{V_{DSATp}}{2} \right)}{1 + r}; r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}} = \frac{\mu_{satp} W_p}{\mu_{satn} W_n}$$

$$V_M \approx \frac{r V_{DD}}{1 + r}; V_{DD} \gg V_T + V_{DSAT}$$

Inverter

Switching Threshold

- V_M where $V_{in} = V_{out}$ (both PMOS and NMOS in saturation since $V_{DS} = V_{GS}$)
 $V_M \approx rV_{DD}/(1 + r)$ where $r = k_p V_{DSATp}/k_n V_{DSATn}$
- Switching threshold set by the ratio r , which compares the **relative driving strengths** of the PMOS and NMOS transistors
- **Want** $V_M = V_{DD}/2$ (to have comparable high and low noise margins), so want $r \approx 1$

Inverter

Switching Threshold As a Function of Transistor Ratio

$$k_n V_{DSATn} \left(V_M - V_{Tn} - \frac{V_{DSATn}}{2} \right) + k_p V_{DSATp} \left(V_M - V_{DD} - V_{Tn} - \frac{V_{DSATn}}{2} \right) = 0$$

$$k = k' \frac{W}{L}$$

$$\frac{(W/L)_p}{(W/L)_n} = \frac{k'_n V_{DSATn} (V_M - V_{Tn} - V_{DSATn}/2)}{k'_p V_{DSATp} (V_{DD} - V_M + V_{Tp} + V_{DSATp}/2)}$$

Inverter

Switching Threshold : Example


0.25μm CMOS
VDD=2.5V L=0.25μm W=0.375μm


	$V_{Th}(V)$	$\gamma(V^{0.5})$	$V_{DSAT}(V)$	$k'(A/V^2)$	$\lambda(V^{-1})$
NMOS	0.43	0.4	0.63	$115 \cdot 10^{-6}$	0.06
PMOS	-0.4	-0.4	-1	$-30 \cdot 10^{-6}$	-0.1

$$\frac{(W/L)_p}{(W/L)_n} = \frac{115 \times 10^{-6}}{30 \times 10^{-6}} \times \frac{0.63}{1.0} \times \frac{(1.25 - 0.43 - 0.63/2)}{(1.25 - 0.4 - 1.0/2)} = 3.5$$

$$(W/L)_p = 3.5 \times 1.5 = 5.25 \text{ for a } V_M \text{ of } 1.25V$$

Inverter

 

 

Inverter Gain

$$k_n V_{DSATn} \left(V_M - V_{Tn} - \frac{V_{DSATn}}{2} \right) (1 + \lambda_n V_{out}) +$$
$$k_p V_{DSATp} \left(V_M - V_{DD} - V_{Tn} - \frac{V_{DSATn}}{2} \right) (1 + \lambda_p V_{out} - \lambda_p V_{DD}) = 0$$
$$g = \frac{dV_{out}}{dV_{in}}$$
$$g = - \frac{1}{I_D(V_M)} \frac{k_n V_{DSATn} + k_p V_{DSATp}}{\lambda_n - \lambda_p} \approx \frac{1+r}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$$

Inverter

Inverter Gain : Example 0.25µm CMOS

VDD=2.5V L=0.25µm W=0.375µm

	V _{TH} (V)	γ(V ^{0.5})	V _{DSAT} (V)	k'(A/V ²)	λ(V ⁻¹)
NMOS	0.43	0.4	0.63	115.10 ⁻⁶	0.06
PMOS	-0.4	-0.4	-1	-30.10 ⁻⁶	-0.1


$I_D(V_M) = 1.5 \times 115 \times 10^{-6} \times (1.25 \times -0.43 - 0.63 / 2)(1 + 0.06 \times 1.25) = 59 \mu A$

$g = \frac{1}{59 \times 10^{-6}} \frac{1.5 \times 115 \times 10^{-6} \times 0.63 + 1.5 \times 3.4 \times 30 \times 10^{-6} \times 1.0}{0.06 + 0.1} = -27.5$

$V_{IL} = 1.2V; V_{IH} = 1.3V; NM_L = NM_H = 1.2V$


Inverter

CMOS Inverter VTC from Simulation

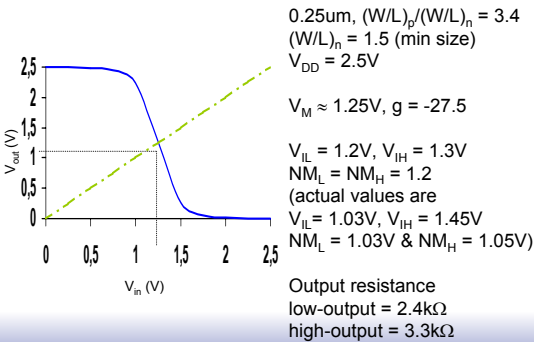



Inverter


Inverter Gain : Example Simulation

 


Inverter

 

 

 

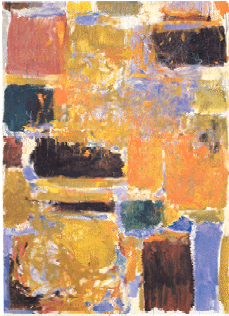


Propagation Delay

Inverter

CMOS Inverter Propagation Delay

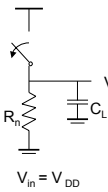□ Propagation delay is proportional to the time-constant of the network formed by the pull-down resistor and the load capacitance





$$t_{pHL} = \ln(2) R_{eqn} C_L = 0.69 R_{eqn} C_L$$
$$t_{pLH} = \ln(2) R_{eqp} C_L = 0.69 R_{eqp} C_L$$
$$t_p = (t_{pHL} + t_{pLH})/2 = 0.69 C_L (R_{eqn} + R_{eqp})/2$$

□ To equalize rise and fall times make the on-resistance of the NMOS and PMOS approximately equal.

Inverter

Equivalent Resistance R_{EQ}

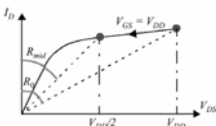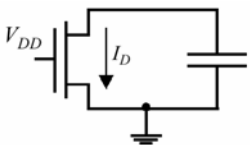

$$R_{eq} = \text{average}_{t_1 \rightarrow t_2} (R_{on}(t)) = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} R_{on}(t) dt = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} \frac{V_{DS}(t)}{I_D(t)} dt$$
$$= \frac{1}{2} (R_{on}(t_1) + R_{on}(t_2))$$

Inverter

Equivalent Resistance R_{EQ}

Solving the integral:

$$R_{eq} = \frac{1}{-V_{DD}/2} \int_{V_{DD}}^{V_{DD}/2} \frac{V'}{I_{DSAT}(1 + \lambda V')} dV' = \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{7}{9} \lambda V_{DD}\right)$$

with appropriately calculated I_{dsat}


$$I_{DSAT} = k \cdot \frac{W}{L} \left((V_{DD} - V_T) V_{DSAT} - \frac{V_{DSAT}^2}{2} \right)$$

Averaging resistances:

$$R_{eq} = \frac{1}{2} \left(\frac{V_{DD}}{I_{DSAT}(1 + \lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT}(1 + \lambda V_{DD}/2)} \right) = \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{5}{6} \lambda V_{DD}\right)$$

Inverter

Equivalent Resistance R_{EQ}

 

$W/L=1, L=0.25\mu$

$V_{DD}(V)$	1	1.5	2	2.5
NMOS (k Ω)	35	19	15	13
PMOS (k Ω)	115	55	38	31

Inverter


Propagation Delay


$$t_{pHL} = \ln(2) R_{eqn} C_L = 0.69 R_{eqn} C_L$$

$$t_{pLH} = \ln(2) R_{eqp} C_L = 0.69 R_{eqp} C_L$$

$$t_p = \frac{t_{pHL} + t_{pLH}}{2} = 0.69 C_L \left(\frac{R_{eqn} + R_{eqp}}{2} \right)$$

Inverter

 

 

Design for Performance

- Reduce C_L
 - internal diffusion capacitance of the gate itself
 - keep the drain diffusion as small as possible
 - interconnect capacitance
 - fanout
- Increase W/L ratio of the transistor
 - the most powerful and effective performance optimization tool in the hands of the designer
 - watch out for self-loading! – when the intrinsic capacitance dominates the extrinsic load
- Increase V_{DD}
 - can trade-off energy for performance
 - increasing V_{DD} above a certain level yields only very minimal improvements
 - reliability concerns enforce a firm upper bound on V_{DD}


Inverter

NMOS/PMOS Ratio

- So far have sized the PMOS and NMOS so that the R_{eq} 's match (ratio of 3 to 3.5)
 - symmetrical VTC
 - equal high-to-low and low-to-high propagation delays

Inverter

NMOS/PMOS Ratio

 

$$C_L = (C_{dp1} + C_{dn1}) + (C_{gp2} + C_{gn2}) + C_W$$

Inverter

NMOS/PMOS Ratio

$$\beta = \frac{(W/L)_p}{(W/L)_n}$$
$$C_L = (1 + \beta)(C_{dn1} + C_{gn2}) + C_W$$
$$t_p = \frac{0.69}{2}((1 + \beta)(C_{dn1} + C_{gn2}) + C_W) \left(R_{eqn} + \frac{R_{eqp}}{\beta} \right)$$
$$t_p = 0.345((1 + \beta)(C_{dn1} + C_{gn2}) + C_W) R_{eqn} \left(1 + \frac{r}{\beta} \right)$$
$$\beta = \beta_{opt} \rightarrow \frac{\partial t_p}{\partial \beta} = 0$$
$$\beta_{opt} = \sqrt{r \left(1 + \frac{C_W}{C_{dn1} + C_{gn2}} \right)} \approx \sqrt{r}$$


Inverter

NMOS/PMOS Ratio

- If speed is the only concern, **reduce** the width of the PMOS device!
 - widening the PMOS degrades the t_{pHL} due to larger parasitic capacitance
$$\beta = (W/L_p)/(W/L_n)$$
$$r = R_{eqp}/R_{eqn} \text{ (resistance ratio of identically-sized PMOS and NMOS)}$$
$$\beta_{opt} = \sqrt{r} \text{ when wiring capacitance is negligible}$$

Inverter

NMOS/PMOS Ratio

 

Inverter

Device Sizing for Performance

- Divide capacitive load, C_L , into
 - C_{int} : intrinsic - diffusion and Miller effect
 - C_{ext} : extrinsic - wiring and fanout
$$t_p = 0.69 R_{eq} C_{int} (1 + C_{ext}/C_{int})$$
$$= t_{p0} (1 + C_{ext}/C_{int})$$
 - where $t_{p0} = 0.69 R_{eq} C_{int}$ is the intrinsic (**unloaded**) delay of the gate

Inverter

Device Sizing for Performance


- Widening both PMOS and NMOS by a factor **S** reduces R_{eq} by an identical factor ($R_{eq} = R_{ref}/S$), but raises the **intrinsic** capacitance by the same factor ($C_{int} = SC_{iref}$)

$$t_p = 0.69 R_{ref} C_{iref} (1 + C_{ext}/(SC_{iref}))$$
$$= t_{p0}(1 + C_{ext}/(SC_{iref}))$$

- t_{p0} is independent of the sizing of the gate; *with no load the drive of the gate is totally offset by the increased capacitance*
- any S sufficiently larger than (C_{ext}/C_{int}) yields the best performance gains with least area impact

Inverter


Device Sizing

 

The majority of the improvement is already obtained for $S = 5$. Sizing factors larger than 10 barely yield any extra gain (and cost significantly more area).

Self-loading effect:
Intrinsic capacitances
dominate

Inverter

 

Inverter Sizing

Inverter


Impact of Fanout on Delay

- Extrinsic capacitance, C_{ext} , is a function of the fanout of the gate - the larger the fanout, the larger the external load.
- First determine the **input loading** effect of the inverter. Both C_g and C_{int} are proportional to the gate sizing, so $C_{int} = \gamma C_g$ is independent of gate sizing and
$$t_p = t_{p0} (1 + C_{ext} / \gamma C_g) = t_{p0} (1 + f / \gamma)$$
i.e., the delay of an inverter is a function of the ratio between its external load capacitance and its input gate capacitance: the **effective fan-out** f
$$f = C_{ext} / C_g$$

Inverter

Inverter Chain

 - Real goal is to minimize the delay through an inverter chain



the delay of the j-th inverter stage is


$$t_{p,j} = t_{p0} (1 + C_{g,j+1} / (\gamma C_{g,j})) = t_{p0} (1 + f_j / \gamma)$$

and
$$t_p = t_{p1} + t_{p2} + \dots + t_{pN}$$

so
$$t_p = \sum t_{p,j} = t_{p0} \sum (1 + C_{g,j+1} / (\gamma C_{g,j}))$$

Inverter

Inverter Chain

 


- If C_L is given:
- How many stages are needed to minimize the delay?
 - How to size the inverters?

May need some additional constraints.

Inverter

Inverter Delay

 - Minimum length devices, $L=0.25\mu\text{m}$
- Assume that for $W_p = 2W_n = 2W$
 - same pull-up and pull-down currents
 - approx. equal resistances $R_N = R_P$
 - approx. equal rise t_{pLH} and fall t_{pHL} delays
- Analyze as an RC network





$$R_P = R_{unit} \left(\frac{W_p}{W_{unit}} \right)^{-1} \approx R_{unit} \left(\frac{W_N}{W_{unit}} \right)^{-1} = R_N = R_W$$

Delay (D): $t_{pHL} = (\ln 2) R_N C_L$ $t_{pLH} = (\ln 2) R_P C_L$

Load for the next stage: $C_{gin} = 3 \times \frac{W}{W_{unit}} C_{unit}$

Inverter



Inverter with Load

  

Assumptions: no load -> zero delay
 $W_{unit} = 1$

Inverter

Inverter with Load

  

Delay = $0.69R_W(C_{int} + C_L) = 0.69R_W C_{int} + 0.69R_W C_L$
= $0.69R_W C_{int}(1 + C_L / C_{int})$
= Delay (Internal) + Delay (Load)

Inverter

Delay Formula


$Delay \sim R_W (C_{int} + C_L)$

$t_p = 0.69 R_W C_{int} (1 + C_L / C_{int}) = t_{p0} (1 + f / \gamma)$

$C_{int} = \gamma C_g$ with $\gamma \approx 1$
 $f = C_L / C_g$ - effective fanout
 $R = R_{unit} / W$; $C_{int} = W C_{unit}$
 $t_{p0} = 0.69 R_{unit} C_{unit}$

Inverter

Apply to Inverter Chain

 

$t_p = t_{p1} + t_{p2} + \dots + t_{pN}$

$t_{pj} \sim R_{unit} C_{unit} \left(1 + \frac{C_{g,j+1}}{\gamma C_{g,j}} \right)$

$t_p = \sum_{j=1}^N t_{p,j} = t_{p0} \sum_{i=1}^N \left(1 + \frac{C_{g,i+1}}{\gamma C_{g,i}} \right), C_{g,N+1} = C_L$

Inverter

Optimal Tapering for Given N

Delay equation has $N - 1$ unknowns, $C_{g,2} - C_{g,N}$

Minimize the delay, find $N - 1$ partial derivatives $\partial t_p / \partial C_{g,j} = 0$

Result: $C_{g,j+1} / C_{g,j} = C_{g,j} / C_{g,j-1}$

Size of each stage is the geometric mean of two neighbors

$C_{g,j} = \sqrt{C_{g,j-1} C_{g,j+1}}$

- each stage has the same effective fanout (C_{out} / C_{in})
- each stage has the same delay

Inverter

Optimum Delay & Number of Stages

When each stage is sized by f and has same eff. fanout f .

$$f^N = F = C_L / C_{gin,1}$$

Effective fanout of each stage:

$$f = \sqrt[N]{F}$$


Minimum path delay

$$t_p = N t_{p0} \left(1 + \sqrt[N]{F} / \gamma \right)$$

The relationship between t_p and F is linear for one inverter, square root for two, etc.

Inverter

Example

 

C_L / C_1 has to be evenly distributed across $N = 3$ stages:

$$C_L / C_{g,1} = 8/1$$

$$f = \sqrt[3]{8} = 2$$

Inverter

Optimum Number of Stages N

□ What is the optimal value for N given

$$f^N = F = C_L / C_{gin,1} \quad t_p = N t_{p0} \left(1 + \sqrt[N]{F} / \gamma \right)$$

- if the number of stages is too large, the intrinsic delay of the stages becomes dominate
- if the number of stages is too small, the effective fan-out of each stage becomes dominate

For a given load, C_L and given input capacitance C_{in}
Find optimal sizing f

$$C_L = F \cdot C_{in} = f^N C_{in} \quad \text{with} \quad N = \frac{\ln F}{\ln f}$$

Inverter

Optimum Number of Stages N

t_p = N t_{p0} (1 + F^{1/N} / \gamma) = \frac{t_{p0} \ln F}{\gamma} \left(\frac{f}{\ln f} + \frac{\gamma}{\ln f} \right)


\frac{\partial t_p}{\partial f} = \frac{t_{p0} \ln F}{\gamma} \cdot \frac{\ln f - 1 - \gamma / f}{\ln^2 f} = 0

For \gamma = 0, f = e, N = \ln F

f = \exp(1 + \gamma / f)

Inverter

Optimum Effective Fanout f

 

- Choosing \gamma larger than optimum has little effect on delay and reduces the number of stages (and area).
 - Common practice to use f = 4 (for \gamma = 1)
 - But too many stages has a substantial negative impact on delay

Inverter

Normalized delay function of F


t_{opt} / t_{p0}

F (\gamma = 1)	Unbuffered	Two Stage Chain	Opt. Inverter Chain
10	11	8.3	8.3
100	101	22	16.5
1,000	1001	65	24.8
10,000	10,001	202	33.1

- Impressive speed-ups with optimized cascaded inverter chain for very large capacitive loads.

Inverter


Buffer Design

 

Inverter

Input Signal Rise/Fall Time

 - In reality, the **input** signal changes gradually (and both PMOS and NMOS conduct for a brief time). This affects the current available for charging/discharging CL and impacts propagation delay.
- tp increases **linearly** with increasing input slope, ts, once ts > ts0
- ts is due to the limited driving capability of the preceding gate



Inverter


Design Challenge

- A gate is never designed in isolation: its performance is affected by both the fan-out and the driving strength of the gate(s) feeding its inputs.
$$t_p = t_{step}^i + \eta t_{step}^{i-1} \quad (\eta \approx 0.25)$$
- Keep signal rise times smaller than or equal to the gate propagation delays.
 - good for performance
 - good for power consumption
- Keeping rise and fall times of the signals small and of approximately equal values is one of the major challenges in high-performance designs - **slope engineering**.

Inverter

Delay with Long Interconnects

 - When gates are farther apart, wire capacitance and resistance can no longer be ignored.



$$t_p = 0.69R_{dr}C_{int} + (0.69R_{dr}+0.38R_w)C_w + 0.69(R_{dr}+R_w)C_{fan}$$

where $R_{dr} = (R_{eqn} + R_{eqp})/2$
$$= 0.69R_{dr}(C_{int}+C_{fan}) + 0.69(R_{dr}c_w+r_wC_{fan})L + 0.38r_wc_wL^2$$

- Wire delay rapidly becomes the dominate factor (due to the **quadratic term**) in the delay budget for longer wires.

Inverter
